

ELECTRONIC CIRCUITS II

CHAPTER 9.
OP-AMP APPLICATIONS


Constant-gain Multiplier

- One of the most common op-amp circuits is the inverting constant-gain multiplier, which provides a precise gain or amplification.

$$A = -\frac{R_f}{R_1}$$


- A noninverting constant-gain multiplier is provided by the circuit

$$A = 1 + \frac{R_f}{R_1}$$

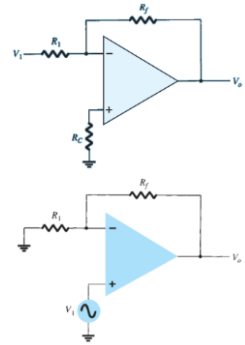

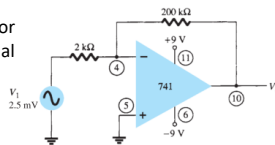EXERCISE

Determine the output voltage for the given circuit with a sinusoidal input of 2.5 mV.



The circuit uses a 741 op-amp to provide a constant or fixed gain,


$$A = -\frac{R_f}{R_1} = -\frac{200 \text{ k}\Omega}{2 \text{ k}\Omega} = -100$$

The output voltage is then


$$V_o = AV_i = -100(2.5 \text{ mV}) = -250 \text{ mV} = -0.25 \text{ V}$$

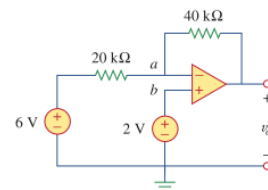EXERCISE

Determine v_o in the op amp circuit shown in Figure.



EXERCISE

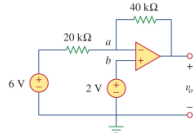

Applying KCL at node a ,

$$\frac{v_a - v_o}{40 \text{ k}\Omega} = \frac{6 - v_a}{20 \text{ k}\Omega}$$

$$v_a - v_o = 12 - 2v_a \Rightarrow v_o = 3v_a - 12$$


But $v_a = v_b = 2 \text{ V}$ for an ideal op amp, because of the zero voltage drop across the input terminals of the op amp. Hence,

$$v_o = 6 - 12 = -6 \text{ V}$$

Notice that if $v_b = 0 = v_a$, then $v_o = -12$, as expected from Eq. (5.9).

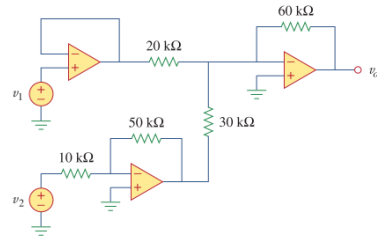
EXERCISE

If $v_1 = 7 \text{ V}$ and $v_2 = 3.1 \text{ V}$, find v_o in the op amp circuit of Fig. 5.33.



Multiple-Stage Gains

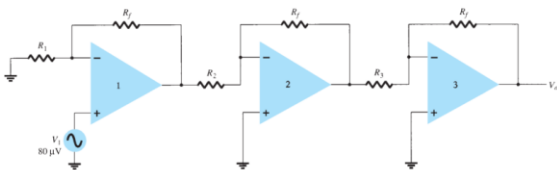- When a number of stages are connected in series, the overall gain is the product of the individual stage gains.



$$A = A_1 A_2 A_3$$

where $A_1 = 1 + R_f/R_1$, $A_2 = -R_f/R_2$, and $A_3 = -R_f/R_3$.

EXERCISE

Show the connection of an LM124 quad op-amp as a three-stage amplifier with gains of +10, -18, and -27.

Use a 270-k Ω feedback resistor for all three circuits.

What output voltage will result for an input of 150 μV ?

EXERCISE

Solution:


For the gain of +10, $A_1 = 1 + \frac{R_f}{R_1} = +10 \Rightarrow R_1 = \frac{R_f}{9} = \frac{270 \text{ k}\Omega}{9} = 30 \text{ k}\Omega$

For the gain of -18, $A_2 = -\frac{R_f}{R_2} = -18 \Rightarrow R_2 = \frac{R_f}{18} = \frac{270 \text{ k}\Omega}{18} = 15 \text{ k}\Omega$

For the gain of -27, $A_3 = -\frac{R_f}{R_3} = -27 \Rightarrow R_3 = \frac{R_f}{27} = \frac{270 \text{ k}\Omega}{27} = 10 \text{ k}\Omega$

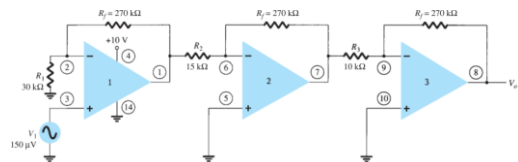EXERCISE

$$V_o = A_1 A_2 A_3 V_1 = 150 \times 10^{-6} \times 10 \times 18 \times 27 = \mathbf{0.729 \text{ V}}$$



EXERCISE

Show the connection of three op-amp stages using an LM348 IC to provide outputs that are -10, -20, and -50 times larger than the input.

Use a feedback resistor of $R_f = 500 \text{ k}\Omega$ in all stages.


EXERCISE

- The resistor component for each stage is calculated to be

$$R_1 = -\frac{R_f}{A_1} = -\frac{500 \text{ k}\Omega}{-10} = 50 \text{ k}\Omega$$


$$R_2 = -\frac{R_f}{A_2} = -\frac{500 \text{ k}\Omega}{-20} = 25 \text{ k}\Omega$$
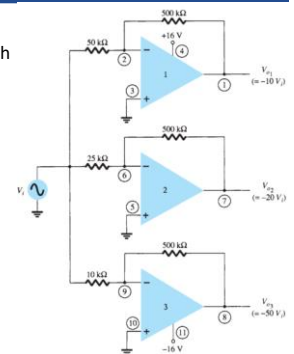
$$R_3 = -\frac{R_f}{A_3} = -\frac{500 \text{ k}\Omega}{-50} = 10 \text{ k}\Omega$$



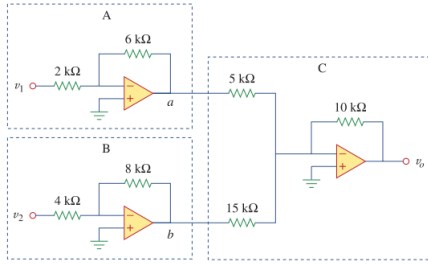
EXERCISE

If $v_1 = 1\text{ V}$ and $v_2 = 2\text{ V}$, find v_o in the given op amp circuit.




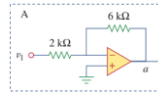EXERCISE


If $v_1 = 1\text{ V}$ and $v_2 = 2\text{ V}$



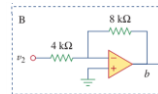The first amplifier of gain:
 $A_1 = -(6\text{ k}\Omega / 2\text{ k}\Omega) = -3v_1 = -3$



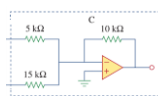The second amplifier of gain:
 $A_2 = -(8\text{ k}\Omega / 4\text{ k}\Omega) = -2v_2 = -4$



The last circuit serves as a summer of two different gains for the output of the other two circuits.


$$V_o = -[(3)(10\text{ k}\Omega / 5\text{ k}\Omega) + (-4)(10\text{ k}\Omega / 15\text{ k}\Omega)]$$

$$V_o = 6 + 2.667 = 8.667\text{ V}$$

Voltage Subtraction


Voltage Subtraction:

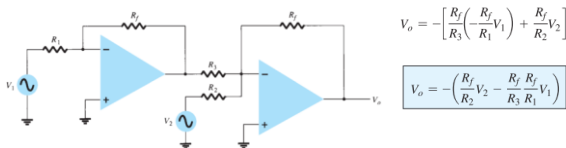- Two signals can be subtracted from one another in a number of ways.
- Figure below shows two op-amp stages used to provide subtraction of input signals using summing circuit.




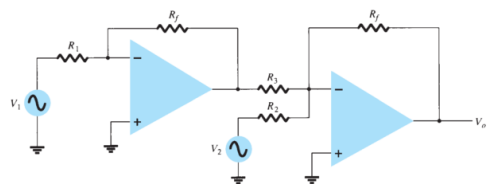EXERCISE

Determine the output for the given circuit with components $R_f = 1\text{ M}\Omega$, $R_1 = 100\text{ k}\Omega$, $R_2 = 50\text{ k}\Omega$, and $R_3 = 500\text{ k}\Omega$.



EXERCISE

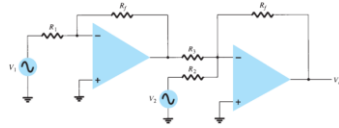

$R_f = 1\text{ M}\Omega$,
 $R_1 = 100\text{ k}\Omega$,
 $R_2 = 50\text{ k}\Omega$, and
 $R_3 = 500\text{ k}\Omega$.

The output voltage is calculated to be:

$$V_o = -\left[\frac{R_f}{R_3} \left(-\frac{R_f}{R_1} V_1 \right) + \frac{R_f}{R_2} V_2 \right]$$

$$V_o = -\left(\frac{R_f}{R_2} V_2 - \frac{R_f R_f}{R_3 R_1} V_1 \right)$$

$$V_o = -\left(\frac{1\text{ M}\Omega}{50\text{ k}\Omega} V_2 - \frac{1\text{ M}\Omega}{500\text{ k}\Omega} \frac{1\text{ M}\Omega}{100\text{ k}\Omega} V_1 \right) = -(20 V_2 - 20 V_1) = -20(V_2 - V_1)$$

EXERCISE


Design an op amp circuit with inputs v_1 and v_2 such that
 $V_o = -5v_1 + 3v_2$.

EXERCISE


$$V_o = -5v_1 + 3v_2 = -(5v_1 - 3v_2)$$

One way to design is to use more than one op amp, we may cascade an inverting amplifier and a two-input inverting summer,
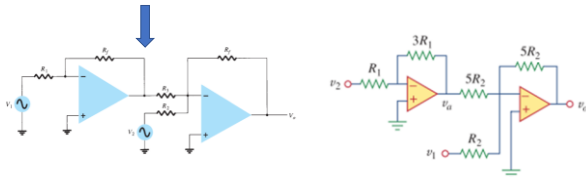
$$V_o = -\left[\frac{R_f}{R_3} \left(\frac{R_f}{R_1} V_1 \right) + \frac{R_f}{R_2} V_2 \right] \Rightarrow \frac{R_f}{R_2} = 5 \quad \text{and} \quad \frac{R_f}{R_3} = 1 \quad \frac{R_f}{R_1} = 3$$



OP-AMP APPLICATIONS

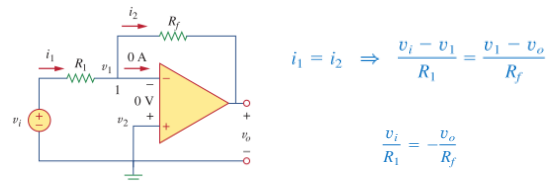

$$i_1 = i_2 \Rightarrow \frac{v_i - v_1}{R_1} = \frac{v_1 - v_o}{R_f}$$

$$\frac{v_i}{R_1} = -\frac{v_o}{R_f}$$

But $v_1 = v_2 = 0$ for an ideal op amp, since the noninverting terminal is grounded. Hence,


$$v_o = -\frac{R_f}{R_1} v_i$$

Voltage Buffer

- A voltage buffer circuit provides a means of isolating an input signal from a load by using a stage having unity voltage gain, with no phase or polarity inversion, and acting as an ideal circuit with very high input impedance and low output impedance.

$$V_o = V_i$$

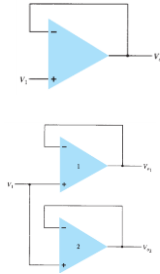- An input signal can be provided as two separate outputs.
- The advantage of this connection is that the load connected across one output has no (or little) effect on the other output.




Controlled Sources

- Operational amplifiers can be used to form various types of controlled sources.
- An input voltage can be used to control an output voltage or current, or an input current can be used to control an output voltage or current.
- These types of connections are suitable for use in various instrumentation

Voltage-Controlled Voltage Source:

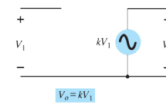
An ideal form of a voltage source whose output V_o is controlled by an input voltage V_i .




Controlled Sources

Voltage-Controlled Voltage Source:

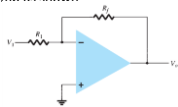This type of circuit can be built using either the inverting input or the noninverting op-amp as shown



$$V_o = -\frac{R_f}{R_1} V_i = kV_i$$


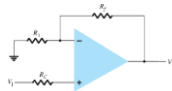


$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_i = kV_i$$

Controlled Sources

Voltage-Controlled Current Source:

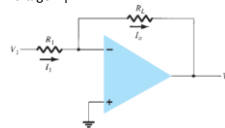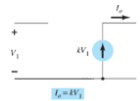- An ideal form of circuit providing an output current controlled by an input voltage is shown.
- The output current is dependent on the input voltage.
- A practical circuit can be built as shown with the output current through load resistor R_L controlled by the input voltage V_i .





$$I_o = \frac{V_i}{R_1} = kV_i$$

Controlled Sources

Current-Controlled Voltage Source:

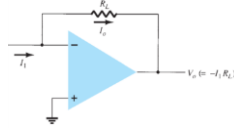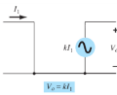- An ideal form of a voltage source controlled by an input current is shown.
- The output voltage is dependent on the input current. A practical form of the circuit is built using an op-amp as shown





$$V_o = -I_i R_L = k I_i$$

Controlled Sources

Current-Controlled Current Source:

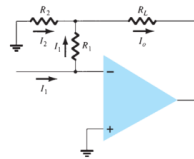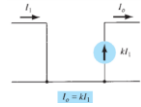- An ideal form of a circuit providing an output current dependent on an input current is shown.
- In this type of circuit, an output current is provided dependent on the input current.
- A practical form of the op-amp circuit is shown.





$$I_o = I_1 + I_2 = I_1 + \frac{I_1 R_1}{R_2} = \left(1 + \frac{R_1}{R_2}\right) I_1 = k I_1$$

ACTIVE FILTERS


- A popular application uses op-amps to build active filter circuits.
- A filter circuit can be constructed using passive components: resistors and capacitors.
- An active filter additionally uses an amplifier to provide voltage amplification and signal isolation or buffering.
- A filter that provides a constant output from dc up to a cutoff frequency f_{OH} and then passes no signal above that frequency is called an ideal **low-pass filter**.
- A filter that provides or passes signals above a cutoff frequency f_{OL} is a **high-pass filter**.
- When the filter circuit passes signals that are above one ideal cutoff frequency and below a second cutoff frequency, it is called a **bandpass filter**.

Low-Pass Filter

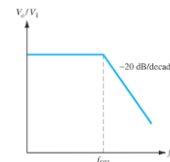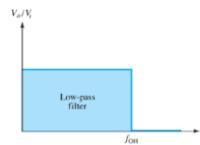
- A first-order, low-pass filter using a single resistor and capacitor is shown in first figure.
- An active filter using op-amp has a practical slope of -20 dB per decade, as shown in second figure.



Low-Pass Filter

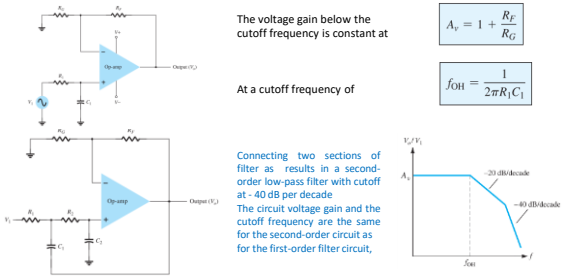

High-Pass Active Filter

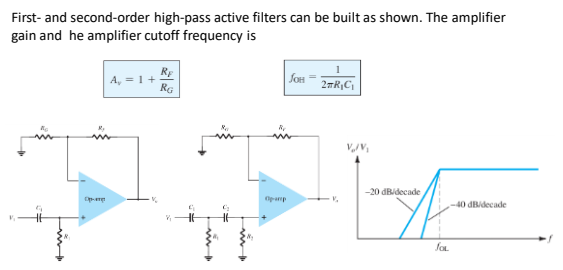

Bandpass Filter

Figure shows a bandpass filter using two stages, the first a high-pass filter and the second a low-pass filter, the combined operation being the desired bandpass response.

